

## Lab 7 Voltage and Circuits

Name: \_\_\_\_\_ Lab Partner(s): \_\_\_\_\_

### Driving Question

You have used electricity throughout your life, but do you know what it is? Electricity can be the sparks and crackling when clothing is pulled apart, and it can be lightning during a storm. It can also be channeled through wires and put to work turning fans, toasting bread, lighting lamps, and connecting you to the world over television, the internet, and phones.

The particles that make up atoms have a property known as charge. It is the presence and motion of these charged particles that gives rise to the phenomenon known as electricity. While we cannot see the charged particles themselves, we are able to investigate how they behave in various devices and materials.

The moving particles in an atom are in the outermost part of the atom's structure and are called electrons. Electrons are about 2000 times smaller than the other particles that make up atoms. Their small size, as well as other factors, makes electrons the easiest part of an atom to push and move. Electrons typically do not move very far or very fast, but very large numbers of them moving at once can deliver a painful shock or heat your home.

Two terms that are often used when discussing electricity are voltage and current. Voltage is a colloquial term for potential difference, which is a way of describing the available energy for electrons to use for moving. The unit used to measure potential difference is the volt (V). Current is the term for the flow of charged particles. In general, the higher the voltage, the more energy is available for electrons to use, and the greater the current. Current is measured in a unit called the ampere (A).

In this experiment, you will have an opportunity to use electricity in small, safe amounts. By investigating how electricity interacts with different objects, you will gradually learn to use electricity effectively to create your own circuits, systems, and devices.

### Objectives

- Detect the presence of current in a wire.
- Explore different types of light bulbs.
- Measure voltage.

### Materials

- Data collection system
- Wireless voltage sensor
- 10- $\Omega$  resistors
- Magnetic compass
- Wires with clips ( $\times 5$ )
- 7.5-V light bulb and socket
- D-cell battery ( $\times 2$ ) and holder
- 3-V coin-cell battery
- LED

**Consider**

1. What is electricity?
2. How do we know electricity is flowing?
3. What conditions are required for electricity to flow?

**Part I: Is Current Present?**

1. Clip several wires together. Place the magnetic compass over the wires as shown in the figure below. Connect the wires to the power supply and observe the compass. Try this several times, moving the orientation of the wire relative to the room each time.



2. Record your observations of how the magnetic compass behaved around the wire.

**Part II: Lighting a Bulb**

1. Obtain a small light bulb. Using a single wire and a single D-cell battery, try different ways of touching them together in order to light the light bulb. You may not cut the wire. Once you determine one way to do it, see if you can find a different way.
2. Brainstorm with your lab partner the variety of ways the light bulb may be made to glow. Draw or otherwise show what to do to light up the bulb. Also, discuss and draw unsuccessful methods. Label your diagrams.

3. Obtain a red LED bulb and a 3-V coin cell battery. Light the LED. Determine a way to always be sure the LED will light.

**Part III: Measuring Voltage in a Circuit**

1. Open *SPARKvue* and build a page with one graph.
2. Connect the wireless voltage sensor. You will use two alligator clip wires connected to the source terminals of the voltage sensor to measure the potential difference between the source terminals.
3. Tare (“zero”) the voltage sensor. Connect the terminals to each other with a wire in order to create a short circuit for taring the sensor. Choose Zero voltage sensor from the Sensors menu. The potential reading  $V$  should be close to zero
4. Insert the two D-cell batteries into the battery holder.
5. Insert the light bulb into the light bulb socket.
6. Connect the wires from the battery holder and the light bulb socket so that the bulb glows.
7. Use the voltage sensor to measure the voltage across each battery individually, the two batteries together, the light bulb, and each wire. Record the voltage values in the table below.
8. Add resistance to the setup. There should be a complete circuit from the batteries to the light bulb to the resistor and back to the batteries. The light bulb should still light, but it may be dimmer than before.
9. Use the voltage sensor to measure the voltage across each battery individually, the two batteries together, the light bulb, the resistor, and each wire. Record the voltage values in the table below.

Component	Potential Difference (V) (Bulb Only)	Potential Difference (V) (Bulb and Resistor)
Battery 1		
Battery 2		
Both batteries together		
Light bulb		
Wire 1		
Wire 2		
Resistor		
Wire 3		

## **Processing Data**

### **Part I: Is Current Present?**

How can you determine whether current is present in a wire?

### **Part II: Lighting a bulb**

Draw a circuit diagram for the wire, light bulb, and battery.

## **Analysis Questions**

1. How would you light a light bulb with only one wire and one battery? Can you do the same with an LED?

2. What are some differences between incandescent light bulbs and LEDs?
3. When you investigated the voltage across various components in a complete circuit, what patterns did you see?

## Extend

1. Add more light bulbs or more resistors to a circuit and investigate if or how the voltage changes.
2. Use the PhET simulation “Circuit Construction Kit” to further explore circuits. To use the PhET simulation, see <http://phet.colorado.edu/en/simulation/circuit-construction-kit-dc>